Norcal 30 High Performance/Low power 30m Transceiver

Dan Tayloe, N7VE

Norcal 30 Novel Features

• High performance Quadrature DC Detector

- High Rcvr Sensitivity/Excellent large signal performance

- Single sided reception with phasing receiver
- 3v low power receiver
- Switching supply minimizes current drain


Norcal 30 Specification Summary

- Receiver Type: Direct Conversion with Phasing
- > 45 db opposite sideband suppression
- Tuning range: 25 KHz, 10.1 10.125 MHz
- Receiver sensitivity: -136.5 dbm (0.1 uV), 3 db S+N/N
- Blocking: > +2 dbm
- Blocking Dynamic Range: > 138 db
- Third order intercept: > +25 IP3
- IM Dynamic Range: > 107 db
- No Spurious SW Broadcast AM Detection
- *Rcvr Blocking/IP3 better than practically useful*

Norcal 30 Specification, Cont.


- Transmit: Variable power, 5w max
- Operating voltage: 12v nominal
- Current drain
 - Receive with moderate signal: 13.5 ma at 12v.
 - 10.5 ma at 16v,
 - 18 ma at 9v
 - Transmit, 5w output: xxx ma at 12v.
- Simple RIT provided (0 to ~800 Hz offset)
- TicK keyer
- SSS Audio Frequency Annunciator

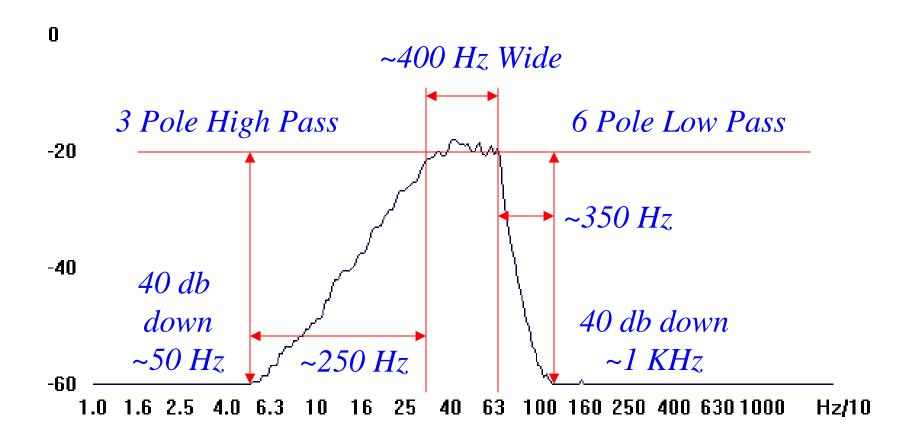Receiver Audio Response Measured Using 30m Band Noise



Two Tone Audio IM Response

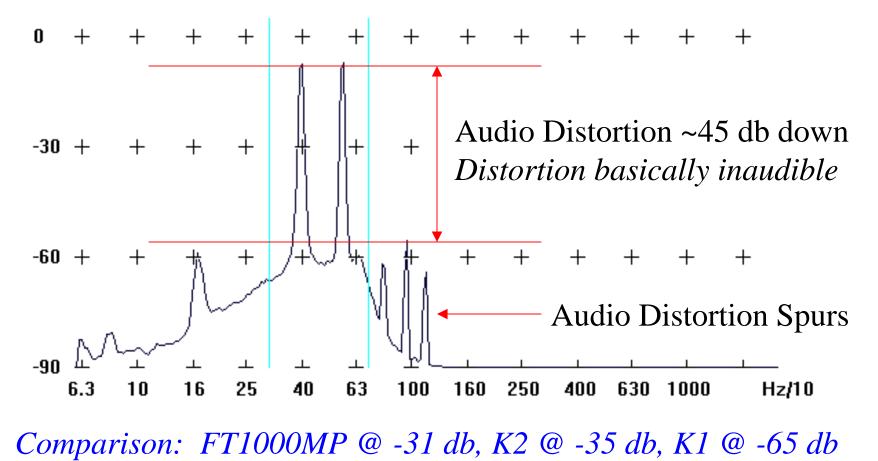Test demonstrates linearity/clarity of the audio chain




Rig Comparisons


- Rig performance data taken from Adventure Radio Society web site.
- The ARS contains a wealth of information comparing the performance of various QRP radios with full size rigs.

www.natworld.com/ars

Receiver Sensitivity

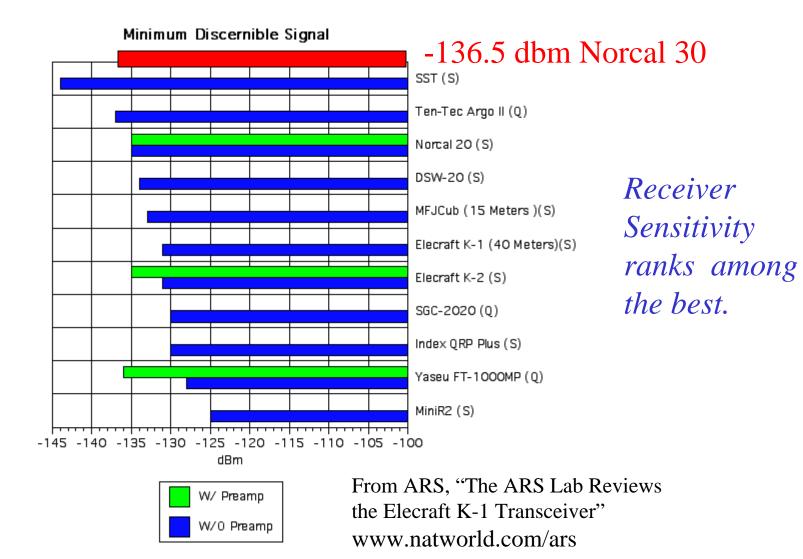


Third Order Dynamic Range

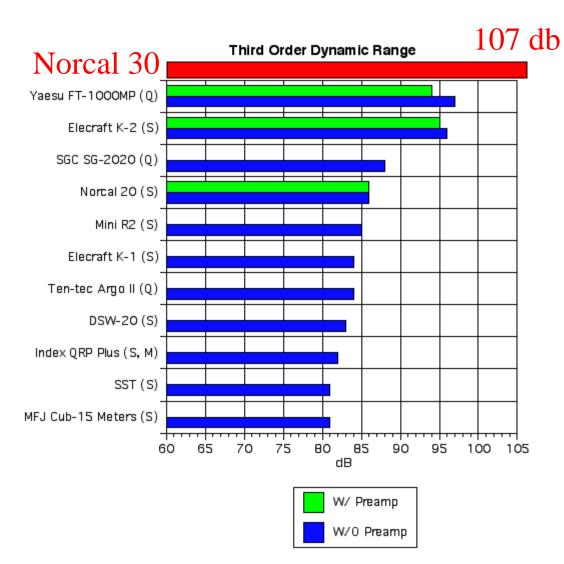


Norcal 30 excels in third order dynamic range.

From ARS, "The ARS Lab Reviews the Elecraft K-1 Transceiver" www.natworld.com/ars

Blocking Dynamic Range

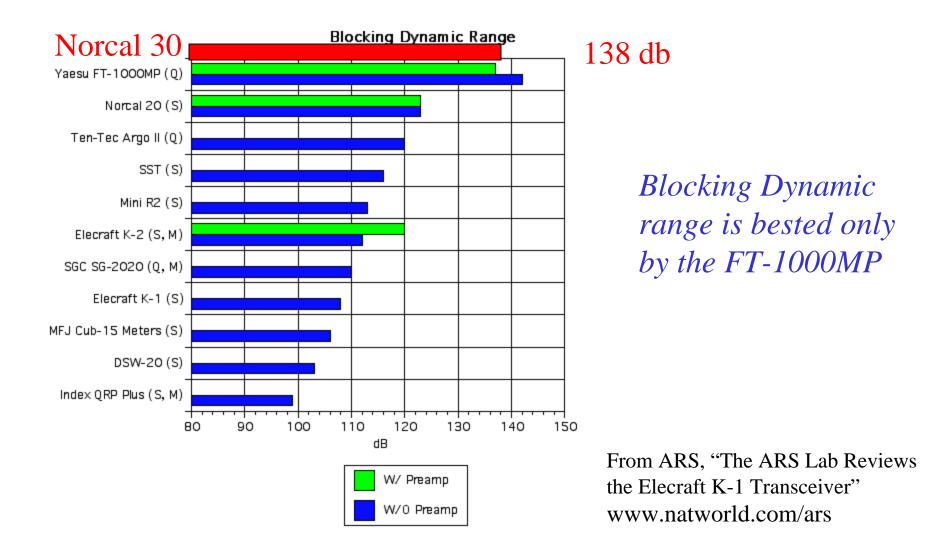

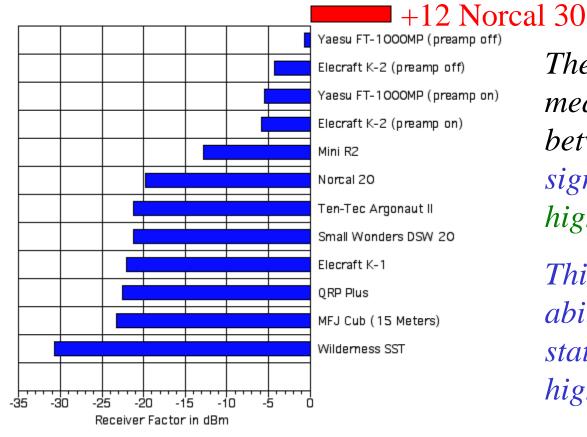ARS – Receiver Factor Sensitivity vs. IP3 Tradeoff



The receiver factor measures the tradeoff between high level signal performance and high sensitivity.

Think of this as the ability to receive weak stations in the midst of high power signals.


From ARS, "The ARS Lab Introduces the Receiver Factor" www.natworld.com/ars

Rcvr Factor = IP3 - NF

How Does Phasing Work?

- Requires quadrature (I & Q) signals as input
 Taken from High Performance Quadrature Detector
- For Norcal 30 USB Signals: I leads Q by 90 degrees
- For Norcal 30 LSB Signals:
 Q leads I by 90 degrees

Picture of Two Sidebands

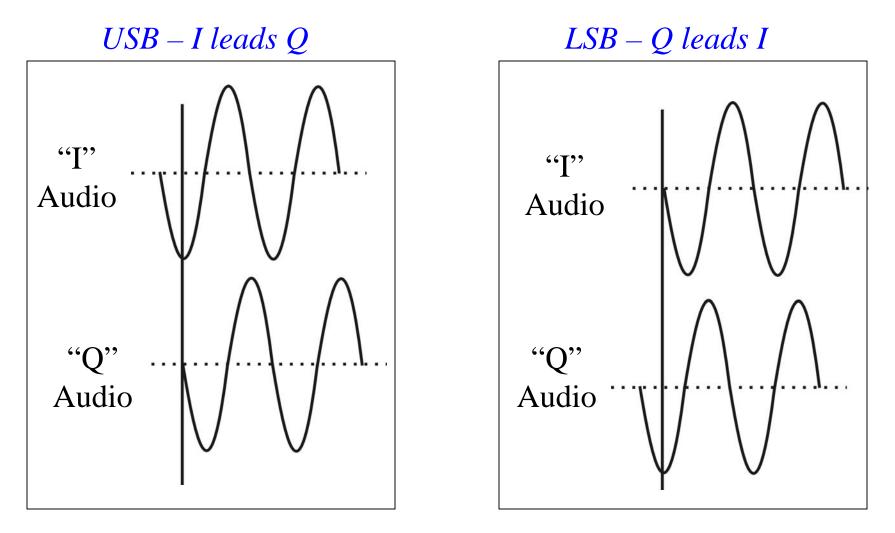


Amplify "As Is" to get a "Binaural" Receiver


Additional 90° Phase Delay Trick

- Trick: Use Phase delay network to add an additional 90° shift between I and Q
- Now LSB I & Q are in phase
- While USB I & Q are 180° out of phase
 After phase shift, LSB signals add while USB


signals cancel.


Before and After - USB

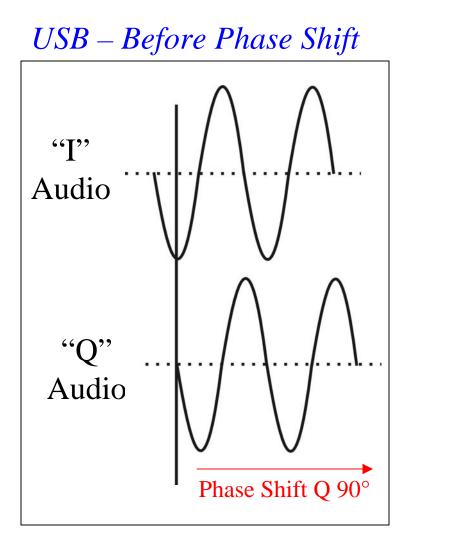

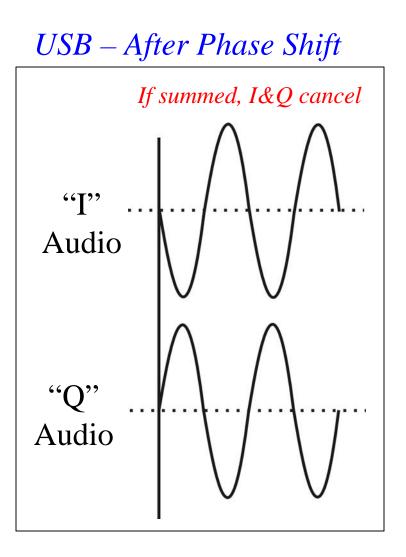

Before and After - LSB

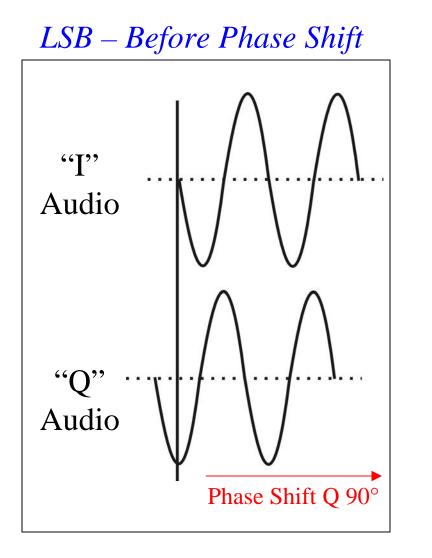


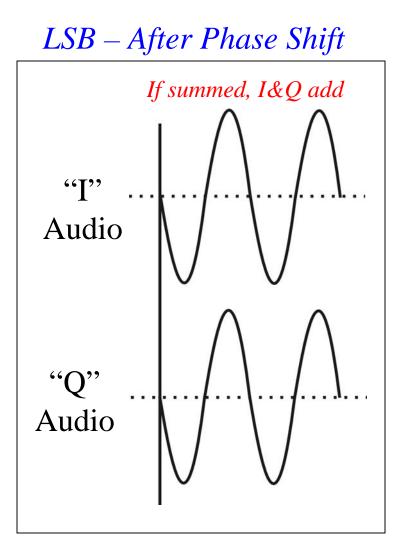

Norcal 30 Phasing Network

- When I/Q audio is applied to the phasing network, the USB sideband cancels out
- Component tolerances non-critical
- Opposite sideband rejection > 45 db
- Sideband rejection set using 3 trim pots
 Balance / Low frequency / High frequency
- Several passes through all three trimmers easily sets opposite sideband rejection

Norcal 30 Phasing Network

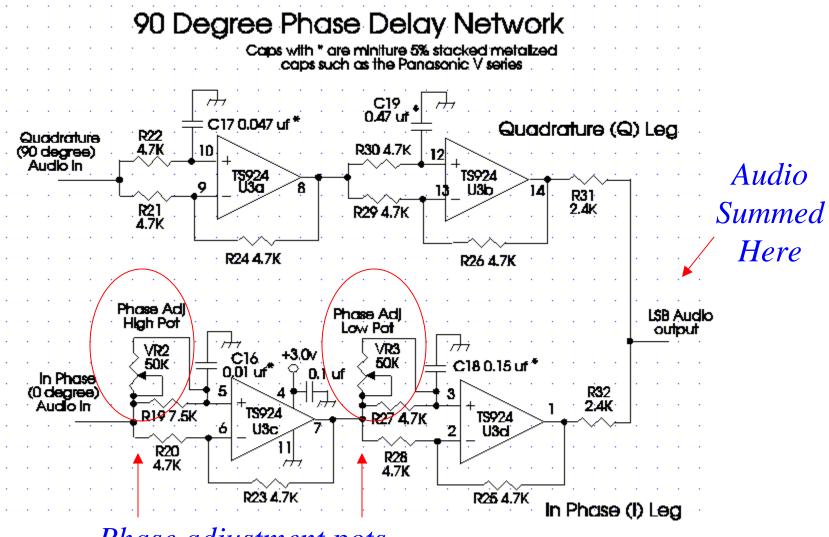

Phase adjustment pots

HB Phasing Strip



Why use a 3v Receiver?

- Goal is to deliver audio signal to the ear.
- Normal headphone listening level is only 100 to 200 mV pk-pk.
- Small, efficient headphones typically rated ~ 40 mW max at 16 ohms.
- 40 mW / 16 ohms is 3.2v pk-pk *But who wants to smoke their headphones?*
- 3v is more than enough for headphones.
- 12v wastes over 9v of battery energy!


Why Use a Switching Supply?

To waste less power when using 12v!

Rough Guidelines


(3 ma at 3v) = (1 ma at 12v)

(2 ma at 5v) = (1 ma at 12v)

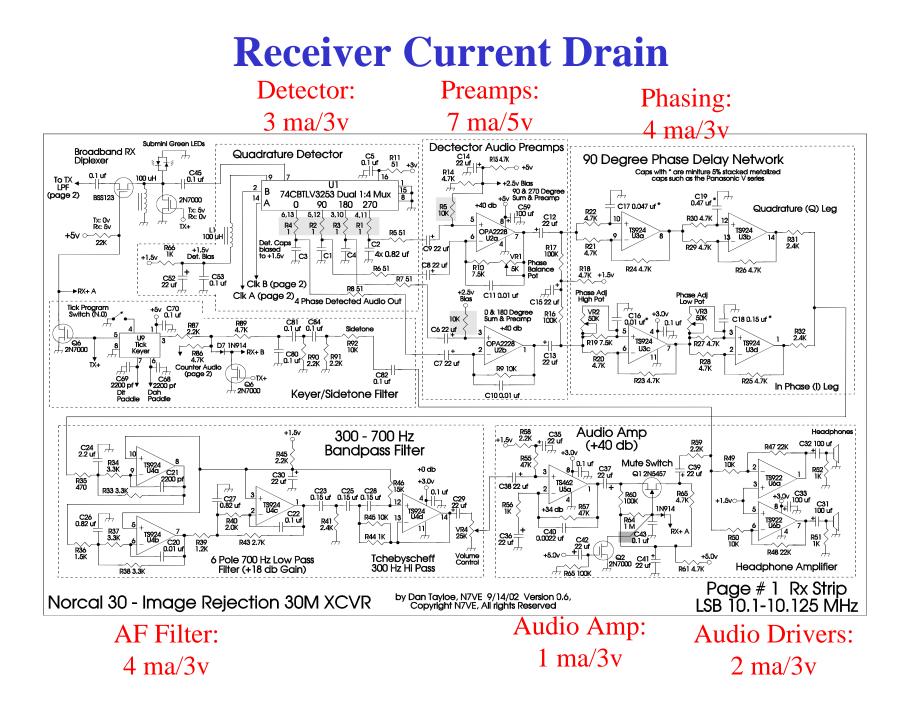

Tripler: 1 ma/3v

VXO: 3 ma/3v

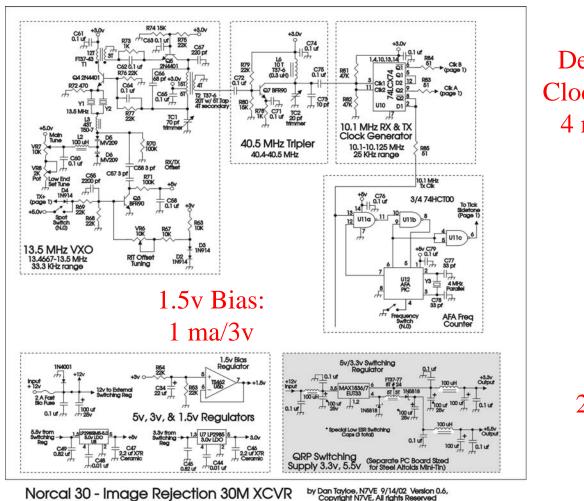

Detector Clock Gen: 4 ma/3v


> Misc.: 2 ma/3v

Grand total: 25 ma, 3v and 7 ma, 5v; ~110 mW

Switching Supply Savings: 32 ma vs. 13 ma

- Total: 25 ma, 3v and 7 ma, 5v; ~110 mW
- Linear LDO Regulators provide clean 3v, 5v
 With 3.3v/5.5v in, LDO regulators burn 10%, 11 mW
- Switching Supply output: 3.3v, 5.5v
 - Switcher circuit is about 75% efficient at 12v
- Switcher: 161 mW in, 121 mW out
- Switcher input, ~13.4 ma at 12v
- If no switching supply: 32 ma
- Switcher saved ~19 ma at 12v.

QRP Switching Power Supply

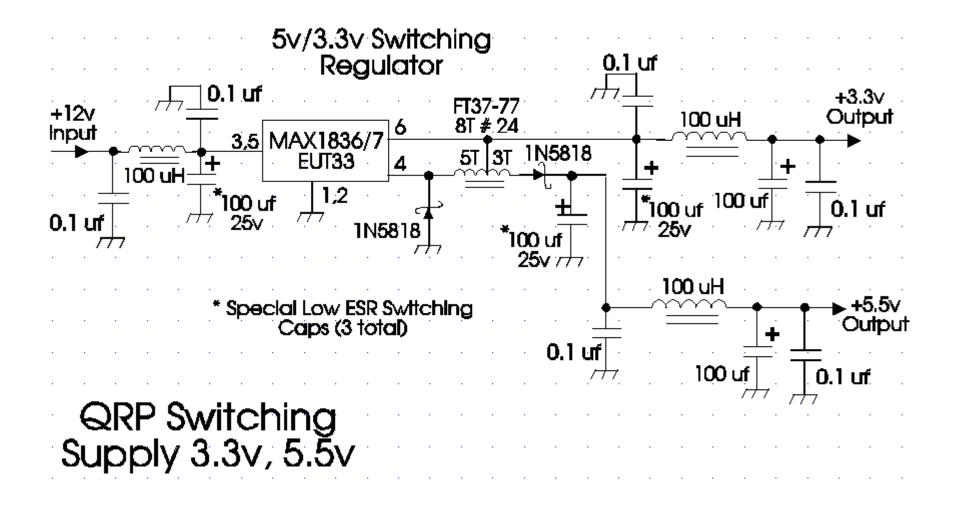

HB QRP Switching Supply



Altoids mini-tin magnetic shielding

Summary: Norcal 30 Design

- High performance Quadrature DC Detector
 - Unmatched Overall Receiver Performance
 - High Rcvr Sensitivity/Excellent large signal performance
- Single sided reception with phasing receiver
 - $> 45 \ db \ of \ USB \ suppression$
- Low power receiver
 - -3v, 110 mW
- Switching supply minimizes current drain
 - Only 13.5 ma at 12v